

Week 6 Workshop Example Solutions

Example 1:

$$H(s) = \frac{\omega_c}{s + \omega_c} = \frac{12,700}{s + 12,700}$$

$$H(j\omega) = \frac{12,700}{12,700 + j\omega}$$

Problem 2:

$$Z_L = j\omega L = j0L = 0 \quad \text{so it is a short circuit.}$$

$$\text{At } \omega = 0, \quad V_o = V_i$$


$$Z_L = j\omega L = j\infty L = \infty \quad \text{so it is an open circuit.}$$

$$\text{At } \omega = \infty, \quad V_o = 0$$

$$H(s) = \frac{V_o}{V_i} = \frac{R}{R + sL} = \frac{R/L}{s + R/L}$$


$$H(s) = \frac{V_o}{V_i} = \frac{R \parallel R_L}{R \parallel R_L + sL} = \frac{\frac{R}{L} \left(\frac{R_L}{R + R_L} \right)}{s + \frac{R}{L} \left(\frac{R_L}{R + R_L} \right)}$$

Problem 3:

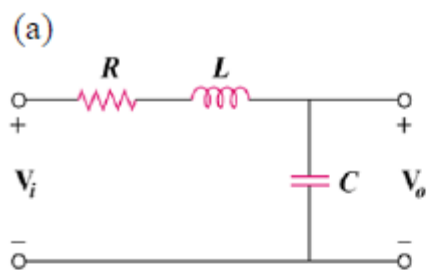

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C}$$
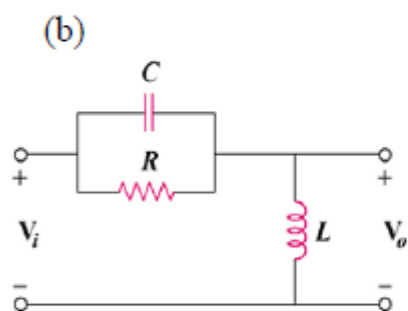
$$= \frac{1}{1 + j\omega RC - \omega^2 LC}$$



$$R \parallel \frac{1}{j\omega C} = \frac{R}{1 + j\omega RC}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{j\omega L}{j\omega L + R/(1 + j\omega RC)} = \frac{j\omega L(1 + j\omega RC)}{R + j\omega L(1 + j\omega RC)}$$

$$= \frac{j\omega L - \omega^2 RLC}{R + j\omega L - \omega^2 RLC}$$

Problem 4:

Refer to notes from the lecture session

Problem 5:

Refer to notes from the lecture session

Problem 6

Refer to notes from the lecture session

Problem 7:

Sketch the Bode plots for



$$G(s) = \frac{s}{(s+2)^2(s+1)}, \quad s = j\omega$$

$$G(\omega) = \frac{(1/4)j\omega}{(1+j\omega)(1+j\omega/2)^2}$$

$$G_{dB} = -20\log_{10} 4 + 20\log_{10}|j\omega| - 20\log_{10}|1+j\omega| - 40\log_{10}|1+j\omega/2|$$


$$\phi = 90^\circ - \tan^{-1}\omega - 2\tan^{-1}\omega/2$$

Magnitude and phase plots

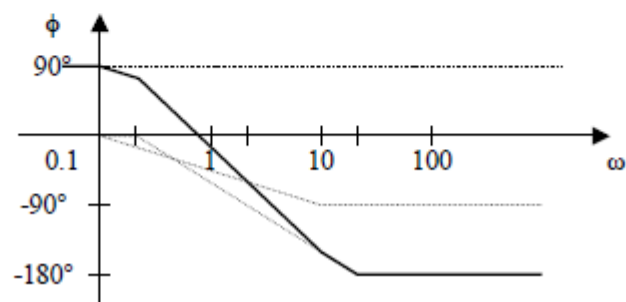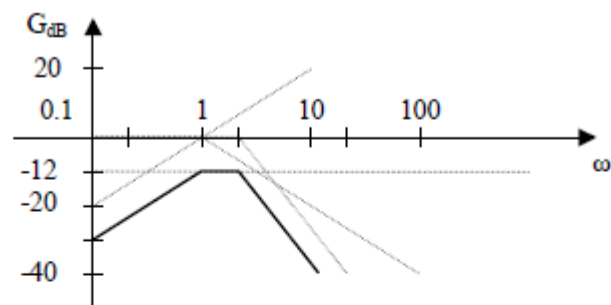

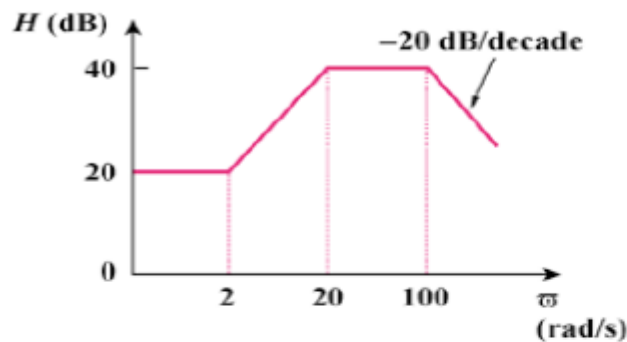Problem 8:

Find the transfer function $H(\omega)$ with the Bode magnitude plot shown



$$20 = 20 \log_{10} k \longrightarrow k = 10$$

A zero of slope +20 dB/dec at $\omega = 2 \rightarrow 1 + j\omega/2$

A pole of slope -20 dB/dec $\omega = 20 \rightarrow \frac{1}{1 + j\omega/20}$

A pole of slope -20 dB/dec at $\omega = 100 \rightarrow \frac{1}{1 + j\omega/100}$

Hence

$$H(\omega) = \frac{10(1 + j\omega/2)}{(1 + j\omega/20)(1 + j\omega/100)}$$