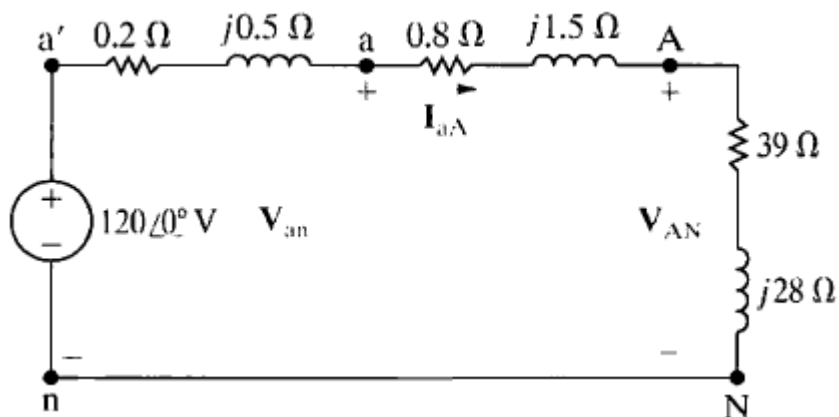


Week 6 Workshop Example Solutions

Example 1:

- $\mathbf{Z}_Y = 50 + j25 = 55.9017 \angle 26.5651^\circ \Omega$, $V_p = V_L / \sqrt{3} = 508.0682 \text{ V}$
- $\mathbf{V}_{an} = 508.0682 \angle 0^\circ$, $\mathbf{V}_{bn} = 508.0682 \angle -120^\circ$, $\mathbf{V}_{cn} = 508.0682 \angle -240^\circ$
- $I_L = V_p / |\mathbf{Z}_Y| = 9.0886 \text{ A}$, $\mathbf{I}_A = I_L \angle -\theta_Y = 9.0886 \angle -26.5651^\circ \text{ A}$, $\mathbf{I}_B = 9.0886 \angle -146.5651^\circ \text{ A}$
- $\mathbf{I}_C = 9.0886 \angle 93.4349^\circ \text{ A}$, $\mathbf{V}_{ab} = 880 \angle 30^\circ \text{ V}$, $\mathbf{V}_{bc} = 880 \angle -90^\circ \text{ V}$, $\mathbf{V}_{ca} = 880 \angle -210^\circ \text{ V}$
- $|\mathbf{S}_L| = V_L I_L = 13852.8883 \text{ VA}$
- $P_L = |\mathbf{S}_L| \cos(\theta_Y) = 12,390.4 \text{ W}$
- $Q_L = |\mathbf{S}_L| \sin(\theta_Y) = 6195.2 \text{ VAR}$
- $\text{pf} = \cos(\theta_Y) = 0.8944272$

Problem 2:

The a-phase line current is

$$\begin{aligned}
 \mathbf{I}_{aA} &= \frac{120 \angle 0^\circ}{(0.2 + 0.8 + 39) + j(0.5 + 1.5 + 28)} \\
 &= \frac{120 \angle 0^\circ}{40 + j30} \\
 &= 2.4 \angle -36.87^\circ \text{ A.}
 \end{aligned}$$

For a positive phase sequence,

$$\mathbf{I}_{bB} = 2.4 \angle -156.87^\circ \text{ A},$$

$$\mathbf{I}_{cC} = 2.4 \angle 83.13^\circ \text{ A}.$$

c) The phase voltage at the A terminal of the load is

$$\begin{aligned}\mathbf{V}_{AN} &= (39 + j28)(2.4 \angle -36.87^\circ) \\ &= 115.22 \angle -11.19^\circ \text{ V}.\end{aligned}$$

For a positive phase sequence,

$$\mathbf{V}_{BN} = 115.22 \angle -121.19^\circ \text{ V},$$

$$\mathbf{V}_{CN} = 115.22 \angle 118.81^\circ \text{ V}.$$

d) For a positive phase sequence, the line voltages lead the phase voltages by 30° ; thus

$$\begin{aligned}\mathbf{V}_{AB} &= (\sqrt{3} \angle 30^\circ) \mathbf{V}_{AN} \\ &= 199.58 \angle 28.81^\circ \text{ V}, \\ \mathbf{V}_{BC} &= 199.58 \angle -91.19^\circ \text{ V}, \\ \mathbf{V}_{CA} &= 199.58 \angle 148.81^\circ \text{ V}.\end{aligned}$$

e) The phase voltage at the a terminal of the source is

$$\begin{aligned}\mathbf{V}_{an} &= 120 - (0.2 + j0.5)(2.4 \angle -36.87^\circ) \\ &= 120 - 1.29 \angle 31.33^\circ \\ &= 118.90 - j0.67 \\ &= 118.90 \angle -0.32^\circ \text{ V}.\end{aligned}$$

For a positive phase sequence,

$$\mathbf{V}_{bn} = 118.90 \angle -120.32^\circ \text{ V},$$


$$\mathbf{V}_{cn} = 118.90 \angle 119.68^\circ \text{ V}.$$

f) The line voltages at the source terminals are

$$\begin{aligned}\mathbf{V}_{ab} &= (\sqrt{3} \angle 30^\circ) \mathbf{V}_{an} \\ &= 205.94 \angle 29.68^\circ \text{ V}, \\ \mathbf{V}_{bc} &= 205.94 \angle -90.32^\circ \text{ V}, \\ \mathbf{V}_{ca} &= 205.94 \angle 149.68^\circ \text{ V}.\end{aligned}$$

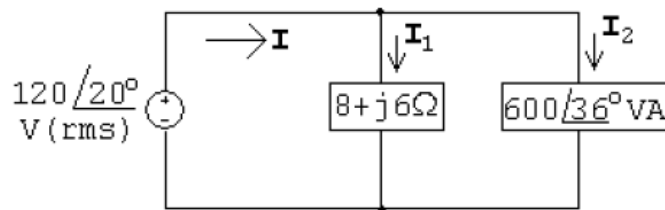Problem 3:

The a-phase of the circuit is shown below:



$$\mathbf{I}_1 = \frac{120\angle 20^\circ}{8 + j6} = 12\angle -16.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_2^* = \frac{600\angle 36^\circ}{120\angle 20^\circ} = 5\angle 16^\circ \text{ A (rms)}$$

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 = 12\angle -16.87^\circ + 5\angle -16^\circ = 17\angle -16.61^\circ \text{ A (rms)}$$

$$S_a = \mathbf{V}\mathbf{I}^* = (120\angle 20^\circ)(17\angle 16.61^\circ) = 2040\angle 36.61^\circ \text{ VA}$$

$$S_T = 3S_a = 6120\angle 36.61^\circ \text{ VA}$$

Problem 4:

The complex power of the source per phase is

$S_s = 20,000 / (\cos^{-1} 0.6) = 20,000 / 53.13^\circ = 12,000 + j16,000$ kVA. This complex power per phase must equal the sum of the per-phase impedances of the two loads:

$$S_s = S_1 + S_2 \quad \text{so} \quad 12,000 + j16,000 = 10,000 + S_2$$

$$\therefore S_2 = 2000 + j16,000 \text{ VA}$$

$$\text{Also, } S_2 = \frac{|V_{\text{rms}}|^2}{Z_2^*}$$

$$|V_{\text{rms}}| = \frac{|V_{\text{load}}|}{\sqrt{3}} = 120 \text{ V (rms)}$$

$$\text{Thus, } Z_2^* = \frac{|V_{\text{rms}}|^2}{S_2} = \frac{(120)^2}{2000 + j16,000} = 0.11 - j0.89 \Omega$$

$$\therefore Z_2 = 0.11 + j0.89 \Omega$$

Problem 5:

$$[\mathbf{a}] \quad \mathbf{I}_{AB} = \frac{13,200 \angle 0^\circ}{100 - j75} = 105.6 \angle 36.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{BC} = 105.6 \angle 156.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{CA} = 105.6 \angle -83.13^\circ \text{ A (rms)}$$

$$[\mathbf{b}] \quad \mathbf{I}_{aA} = \sqrt{3} \angle -30^\circ \mathbf{I}_{AB} = 182.9 \angle 66.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{bB} = 182.9 \angle -173.13^\circ \text{ A (rms)}$$

$$\mathbf{I}_{cC} = 182.9 \angle -53.13^\circ \text{ A (rms)}$$

$$[\mathbf{c}] \quad \mathbf{I}_{ba} = \mathbf{I}_{AB} = 105.6 \angle 36.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{cb} = \mathbf{I}_{BC} = 105.6 \angle 156.87^\circ \text{ A (rms)}$$


$$\mathbf{I}_{ac} = \mathbf{I}_{CA} = 105.6 \angle -83.13^\circ \text{ A (rms)}$$

Problem 6

$$[a] \quad V_{an} = V_{cn} - \underline{120^\circ} = 20 \underline{-210^\circ} = 20 \underline{150^\circ} \text{ V (rms)}$$

$$Z_y = Z_\Delta / 3 = 39 - j33 \, \Omega$$

The a-phase circuit is

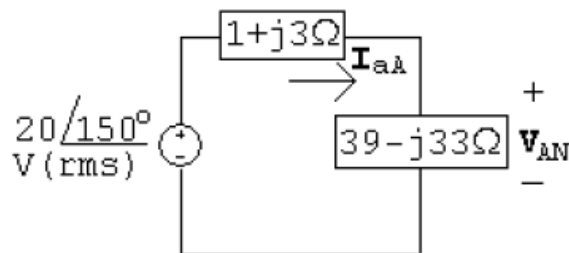

$$[b] \quad I_{aA} = \frac{20 \underline{150^\circ}}{40 - j30} = 0.4 \underline{-173.13^\circ} \text{ A (rms)}$$

$$[c] \quad V_{AN} = (39 + j33)I_{aA} = 20.44 \underline{146.63^\circ} \text{ V (rms)}$$

$$V_{AB} = \sqrt{3} \underline{30^\circ} V_{AN} = 35.39 \underline{176.63^\circ} \text{ A (rms)}$$