



UNIVERSITY
OF WOLLONGONG
IN DUBAI

ECE202: CIRCUITS AND SYSTEMS WEEK 8



UNIVERSITY
OF WOLLONGONG
IN DUBAI




Magnetically Coupled Circuits

Introduction

- Magnetically coupled systems leverage the power of magnetic fields to create efficient and reliable connections between components, enabling seamless energy transfer and communication without direct contact.
- This innovative approach has applications in various fields, including telecommunications, robotics, power transmission, and even medical devices.
- In this session, we will cover the fundamental concepts of magnetism, delve into the different types of magnetic coupling, and discuss their practical applications and advantages over conventional methods.
- I encourage you to engage actively, ask questions, and share your perspectives as we uncover the potential of magnetically coupled systems together. Let's dive in! connected loads have equivalent wye connected loads, and vice versa.

Magnetically Coupled Circuits

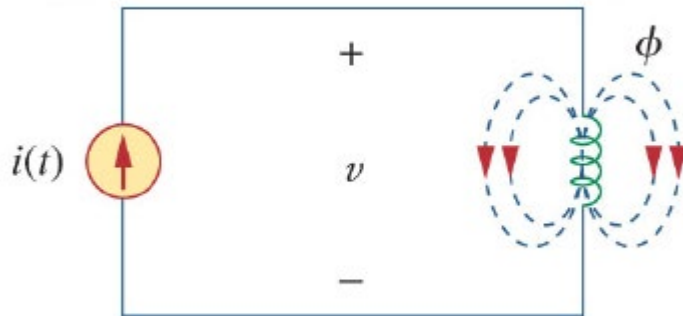- Circuit currents flowing in one mesh, or loop, can be affected by separate currents flowing in adjacent regions, if these are either conductively coupled (common) or magnetically coupled (via mutual inductance).




$$v = N \frac{d\phi}{dt}$$

$$v = N \frac{d\phi}{di} \frac{di}{dt}$$

$$L = N \frac{d\phi}{di}$$

Mutual Inductance

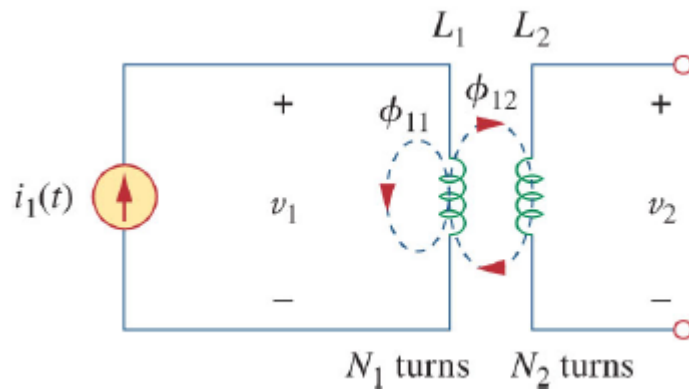- Mutual inductance is the ability of one inductor to induce a voltage across a neighbouring inductor.
- Mutual inductance is measured in Henrys (H).




$$v_1 = N_1 \frac{d\phi_1}{dt} = L_1 \frac{di_1}{dt}$$

$$\phi_1 = \phi_{11} + \phi_{12} \quad v_2 = N_2 \frac{d\phi_{12}}{dt}$$

$$v_2 = N_2 \frac{d\phi_{12}}{di_1} \frac{di_1}{dt} = \boxed{M_{21}} \frac{di_1}{dt}$$

mutual inductance

$$M_{12} = M_{21} = \boxed{M}$$

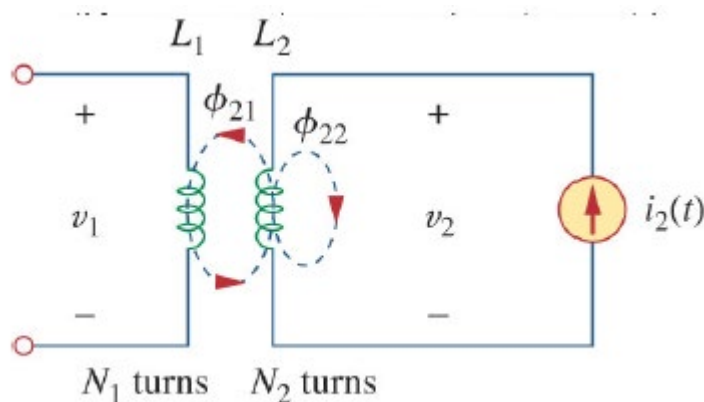


$$v_1 = M_{12} \frac{di_2}{dt}$$







Mutual Inductance

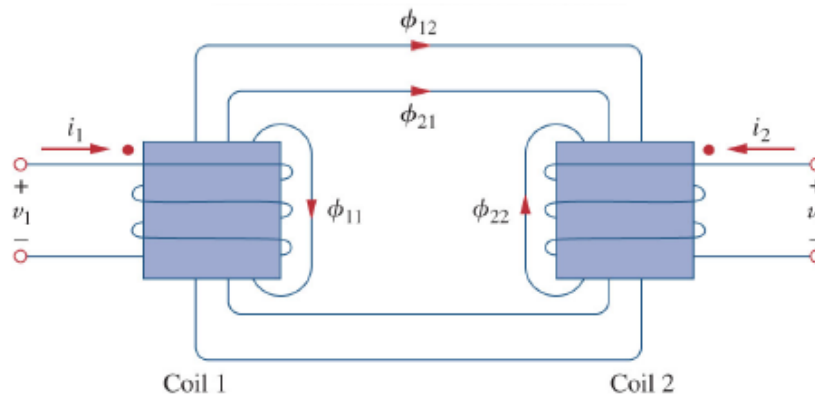- Although mutual inductance is always positive, the resultant mutual voltage ($M di/dt$) may be negative or positive, according to the direction of current flow.




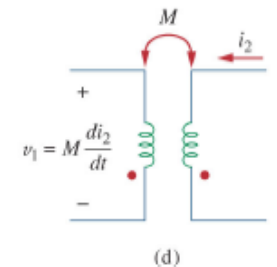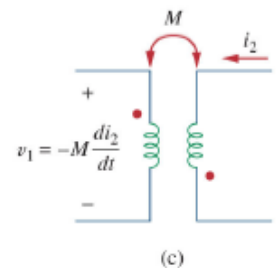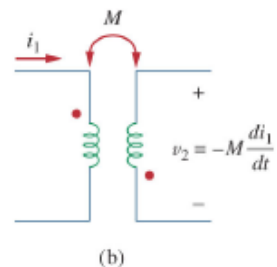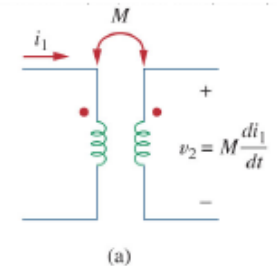Dot convention: if current enters a dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil will be positive at its respective dotted terminal (& vice-versa)




Mutual Inductance


series-aiding

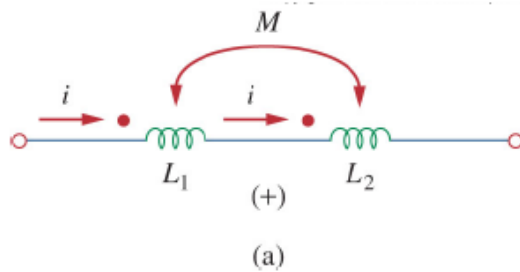

$$L = L_1 + L_2 + 2M$$

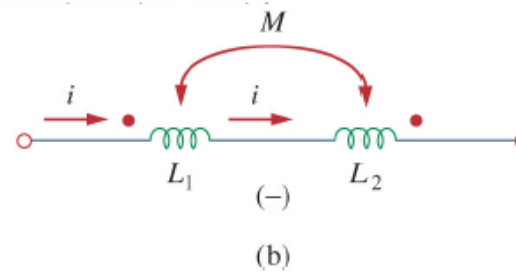


$$L = L_1 + L_2 - 2M$$

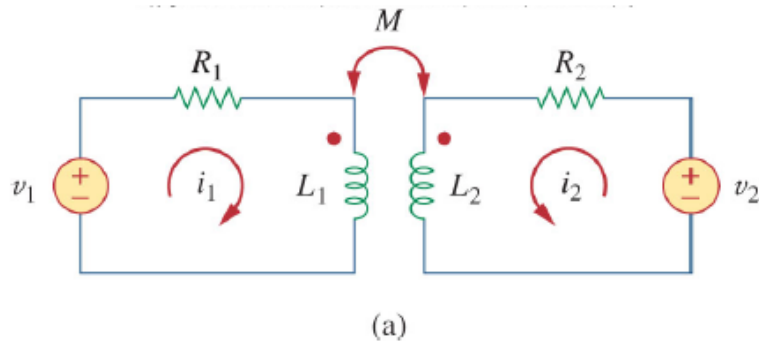

$$V_1 = (R_1 + j\omega L_1)I_1 + j\omega M I_2$$
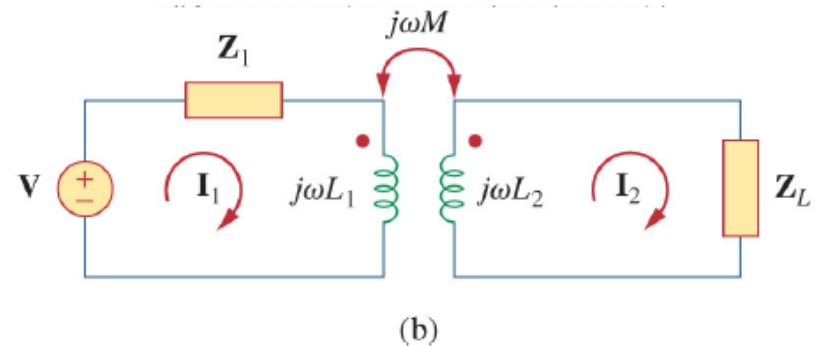
$$V_2 = j\omega M I_1 + (R_2 + j\omega L_2)I_2$$




$$V = (Z_1 + j\omega L_1)I_1 - j\omega M I_2$$

$$j\omega M I_1 = (Z_L + j\omega L_2)I_2$$


Example 1

Find I_1 , I_2 , V_1 , and V_2 in the circuit

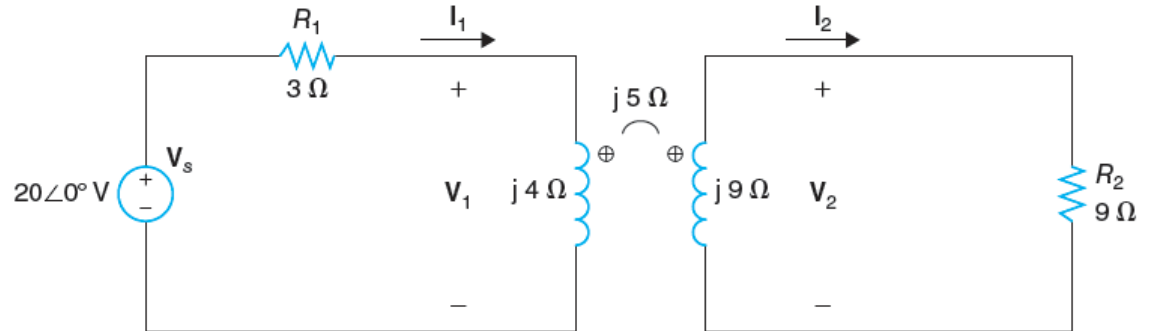


Example 2

Find I_1 , I_2 , and I_3 in the circuit

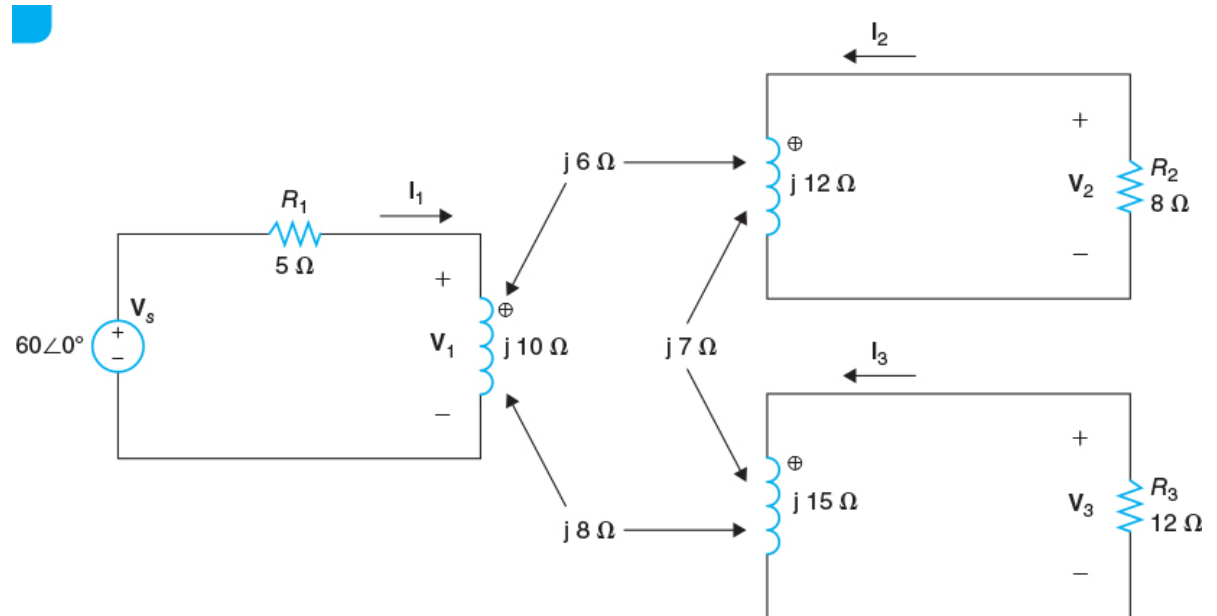

Linear Transformer

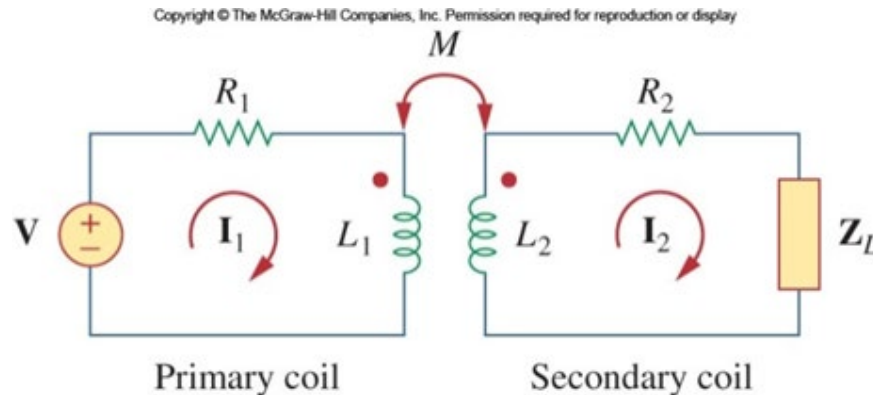- A transformer is a magnetic device that takes advantage of mutual inductance.
- It is generally a four terminal device comprised of two or more magnetically coupled coils.
- The coil that is connected to the voltage source is called the primary, with the one connected to the load called the secondary.
- They are called linear if the coils are wound on a magnetically linear material



Ideal Transformer

- ❖ An ideal transformer is one with perfect coupling.
- ❖ It has two or more windings with a large number of turns on a core of high permeability.
- ❖ The ideal transformer has:
 - ❖ Coils with very large reactance
 - ❖ Coupling coefficient is equal to unity
 - ❖ Primary and secondary coils are lossless
- ❖ Voltages and currents in each winding are related to each other by the turns ratio (n):

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n \qquad \frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$$


- ❖ The impedance that appears at the source is called the reflected impedance:

$$Z_{in} = \frac{Z_L}{n^2}$$

Example 3

In the ideal transformer circuit shown, determine both V_o and the complex power supplied by the source.



Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.

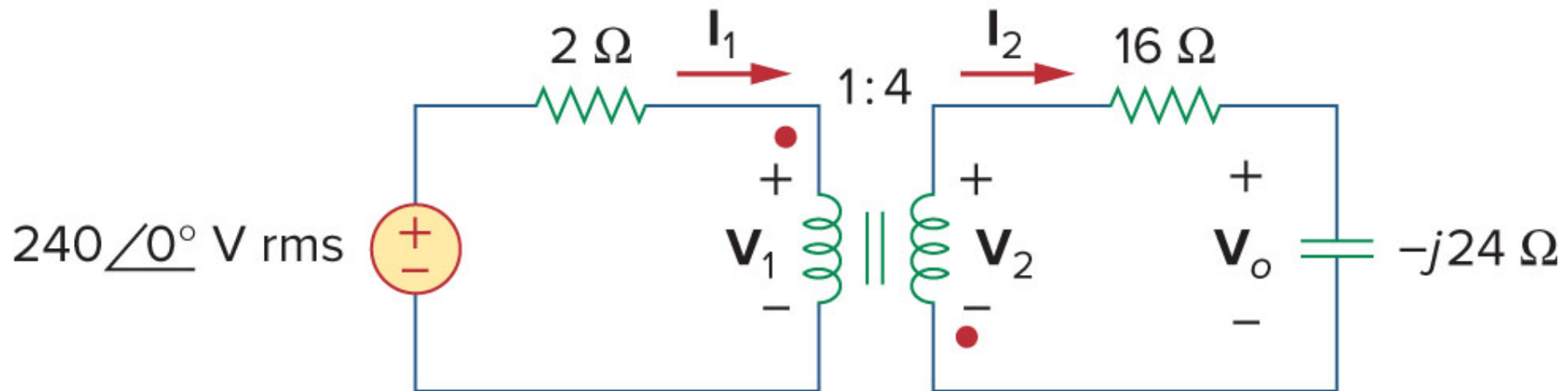

Example 3


Solution

Ideal Transformer-Dot Convention

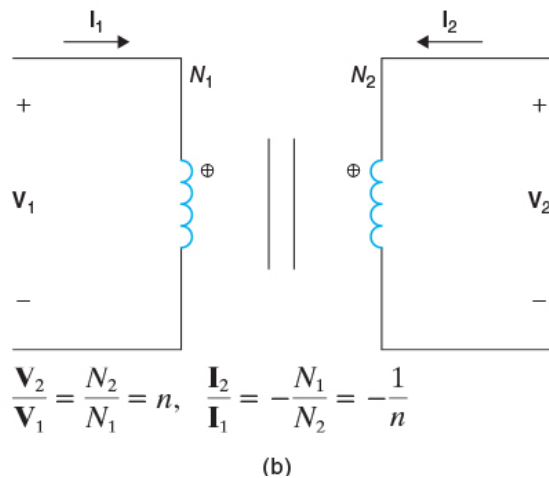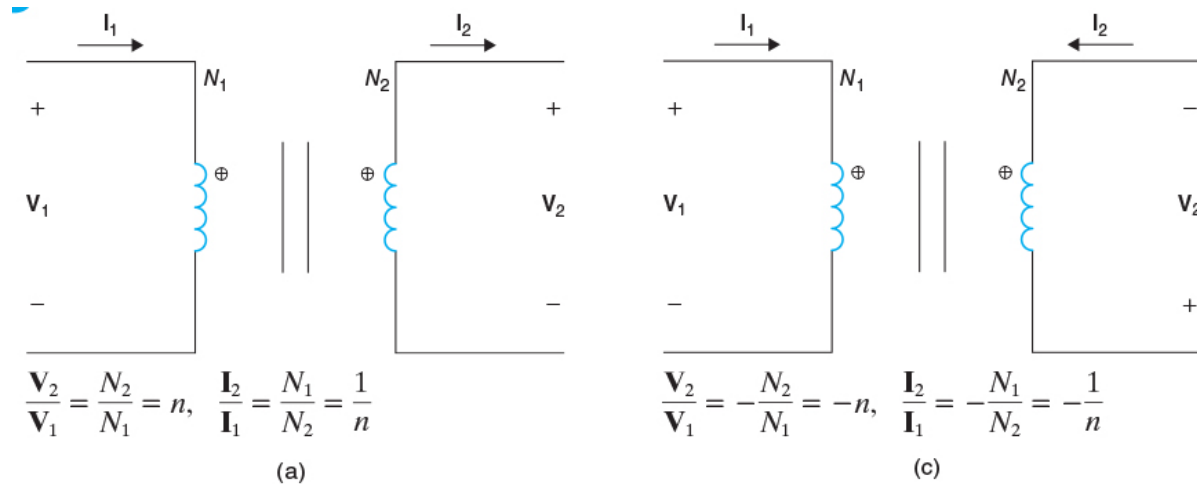

Example 4


Let $\mathbf{V}_s = 70\angle 0^\circ \text{ V}$, $\mathbf{Z}_L = 5 + j3 \Omega$, $n = 1/5$, $\mathbf{Z}_s = 25 + j10 \Omega$ in the circuit below.
Find \mathbf{Z}_{in} , \mathbf{I}_1 , \mathbf{V}_1 , \mathbf{V}_2 , and \mathbf{I}_2 .

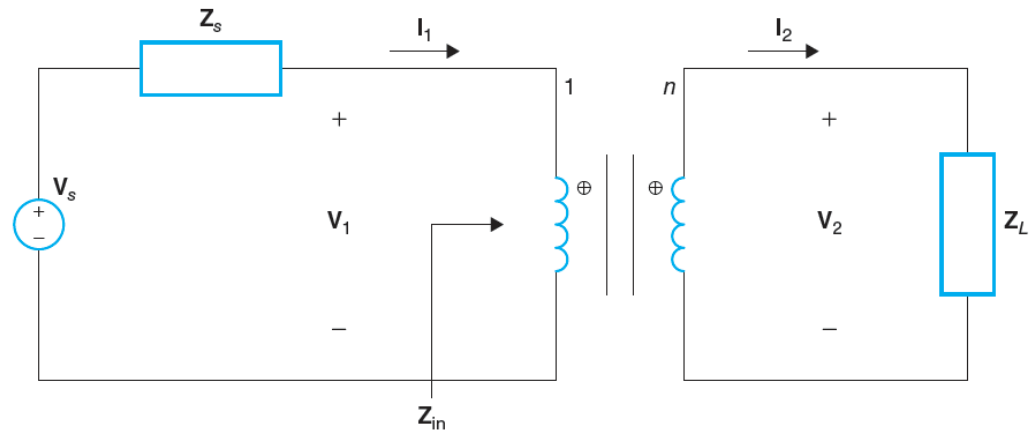

Example 5

The load impedance connected to the secondary winding of the ideal transformer in the figure below consists of a $237.5 \text{ m}\Omega$ resistor in series with a $125 \text{ }\mu\text{H}$ inductor. If the sinusoidal voltage source (V_g) is generating the voltage $2500\cos(400t) \text{ V}$, find the steady-state expressions for:

- a) I_1
- b) V_1
- c) I_2
- d) V_2 .

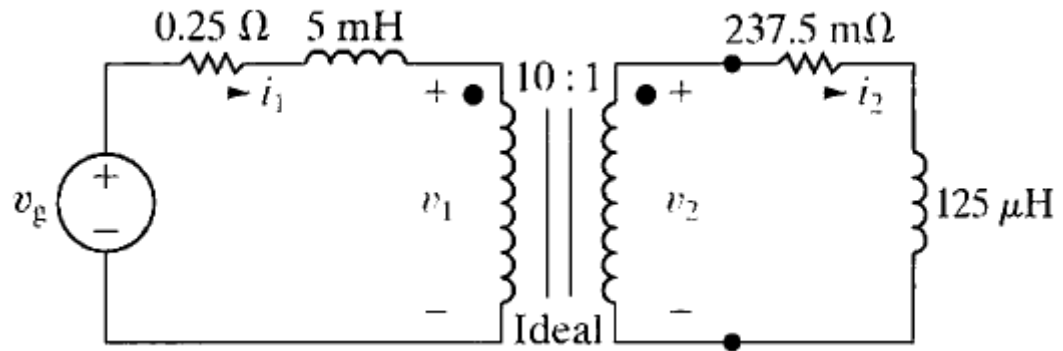


Example 5

Solution



Example 6

The source voltage in the phasor domain circuit in the accompanying figure is 25kV with an angle zero degree. Find the amplitude and phase angle of V_2 and I_2

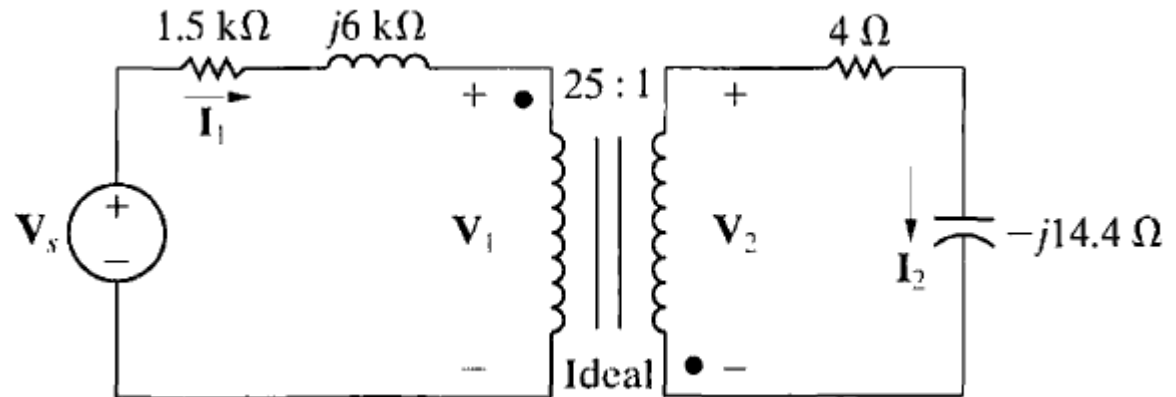

Example 6

Solution