



UNIVERSITY
OF WOLLONGONG
IN DUBAI

ECE202: CIRCUITS AND SYSTEMS WEEK 7



UNIVERSITY
OF WOLLONGONG
IN DUBAI

AC Circuit Frequency Response (Chapter 14)




Three Phase circuit

- In this chapter, circuits connecting balanced three-phase sources and balanced three-phase loads are analyzed.
- The balanced three-phase sources are three voltages with the same amplitude and frequency, but three different phases separated by 120° . The sources can be arranged in a wye (Y) shape or a delta (Δ) shape.
- The balanced loads refer to three loads with identical impedances and also can be arranged in a Y or Δ shape.
- There are four combinations in connecting three-phase sources and three-phase loads.
- These are Y-Y connection, Y- Δ connection, Δ - Δ connection, and Δ -Y connection.
- The delta connected sources have equivalent wye connected sources, and vice versa.
- The delta connected loads have equivalent wye connected loads, and vice versa.




Three Phase

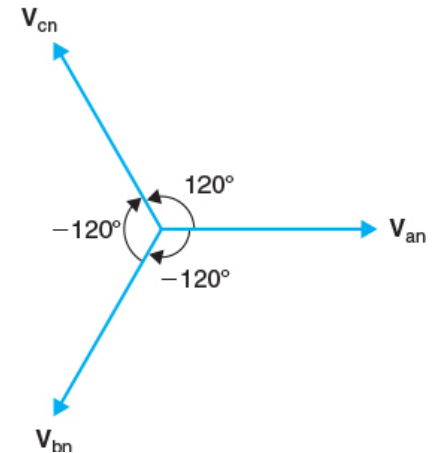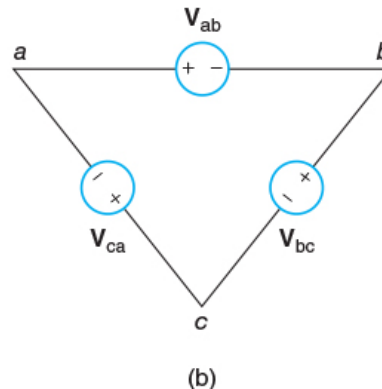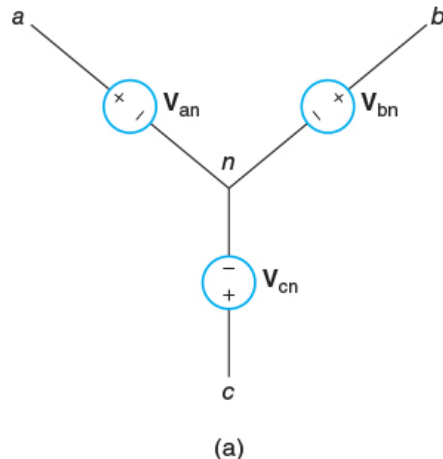- The three voltage sources can be connected in Y shape (wye shape) or Δ shape (delta shape),
- The three voltages V_{an} , V_{bn} , and V_{cn} in the Y-connected source are called phase voltages. $V_{an} + V_{bn} + V_{cn} = 0$.
- The voltages between the lines, V_{ab} , V_{bc} , and V_{ca} , are called line voltages.




Three Phase

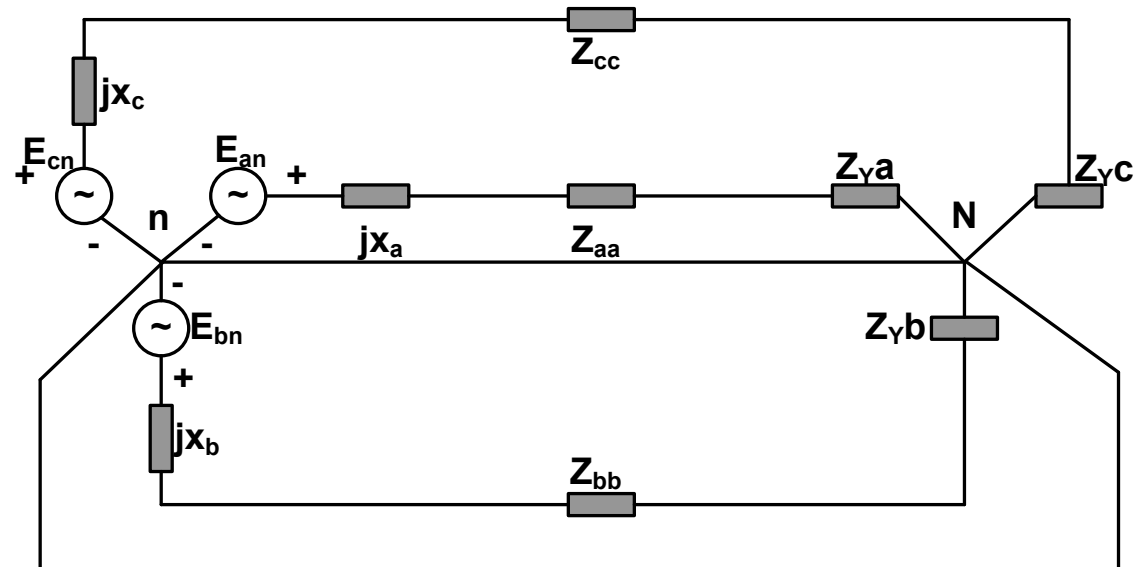- The three voltage sources can be connected to three phase load impedance



Three Phase

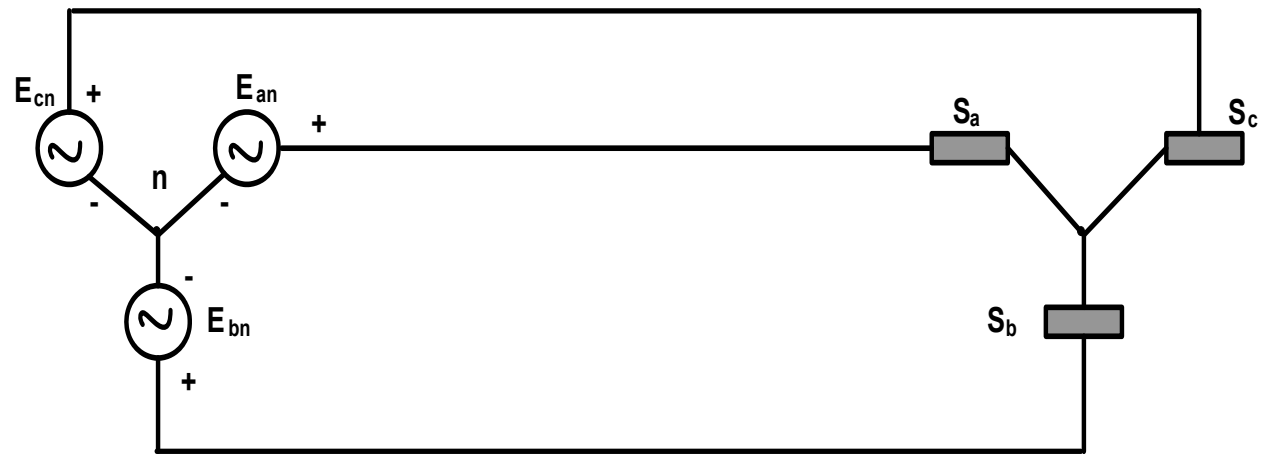- If the 3-phase system is balanced
- The neutral wire doesn't carry any current and it can be omitted from the circuit



Three Phase

- Note that there is the following relationship between phase voltages and line-line voltages:

$$E_{ab} = \sqrt{3}E_{an}\angle 30^\circ$$

$$E_{bc} = \sqrt{3}E_{an}\angle (30-120)^\circ$$

$$E_{ca} = \sqrt{3}E_{an}\angle (30+120)^\circ$$

Assuming the phase 'a' as our reference angle.

Three Phase


- Verify the relation between the line to line voltage and phase voltage

The Basic concepts of power grids: 3 phase systems

$$I_{AB} = \sqrt{3} E_{an} \angle 30^\circ / Z_{\Delta}$$

$$I_{BC} = \sqrt{3} E_{an} \angle (30 - 120)^\circ / Z_{\Delta}$$
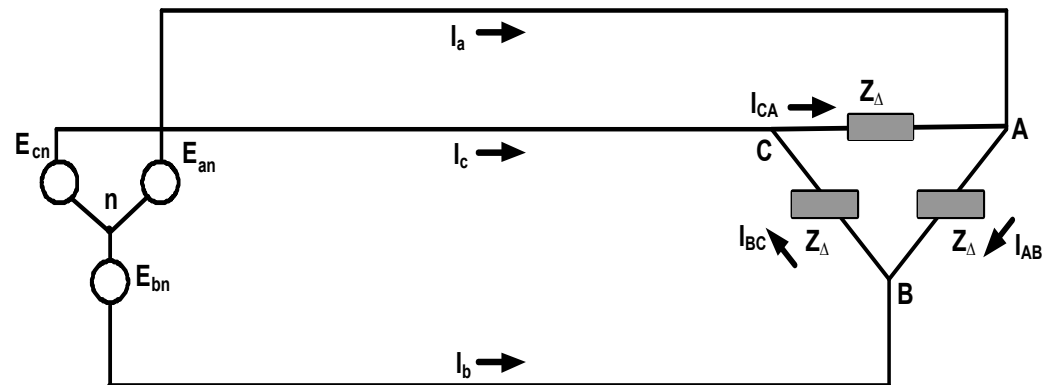
$$I_{CA} = \sqrt{3} E_{an} \angle (30 + 120)^\circ / Z_{\Delta}$$




The Basic concepts of power grids: 3 phase systems

- We have the following relation between line-line current and phase currents:

$$I_a = \sqrt{3}I_{AB} \angle -30^\circ$$



$$I_b = \sqrt{3}I_{BC} \angle -30^\circ$$
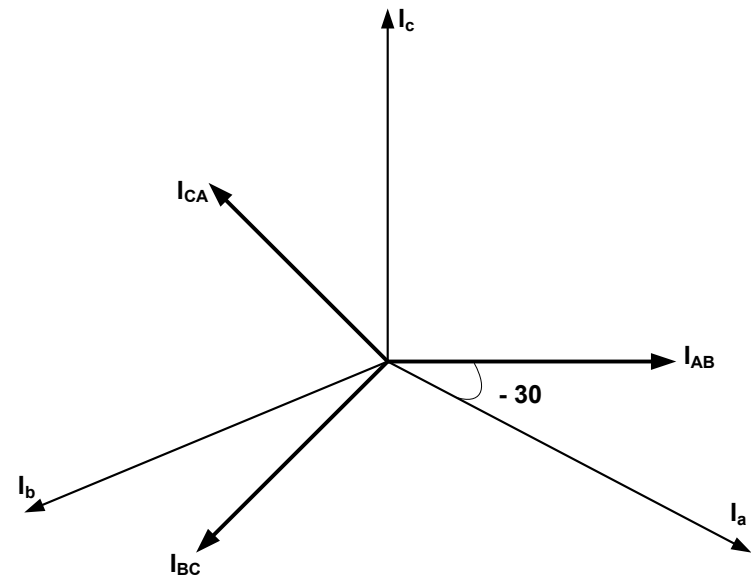
$$I_c = \sqrt{3}I_{CA} \angle -30^\circ$$




The Basic concepts of power grids: 3 phase systems

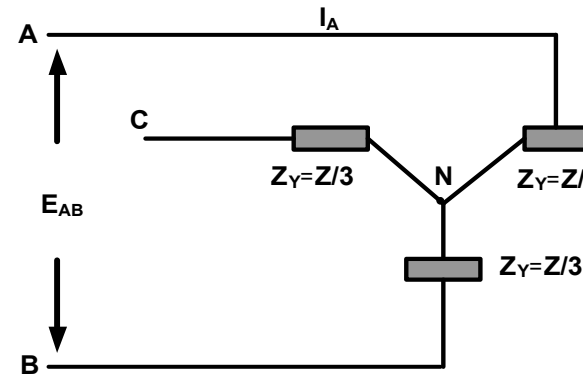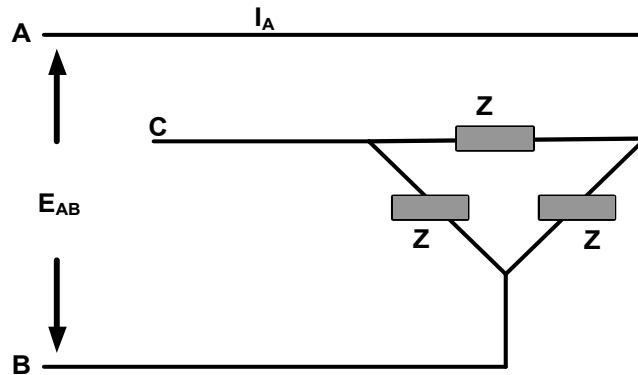Delta connected load could be presented as Y connected load as shown in the figure below:







The Basic concepts of power grids: 3 phase systems

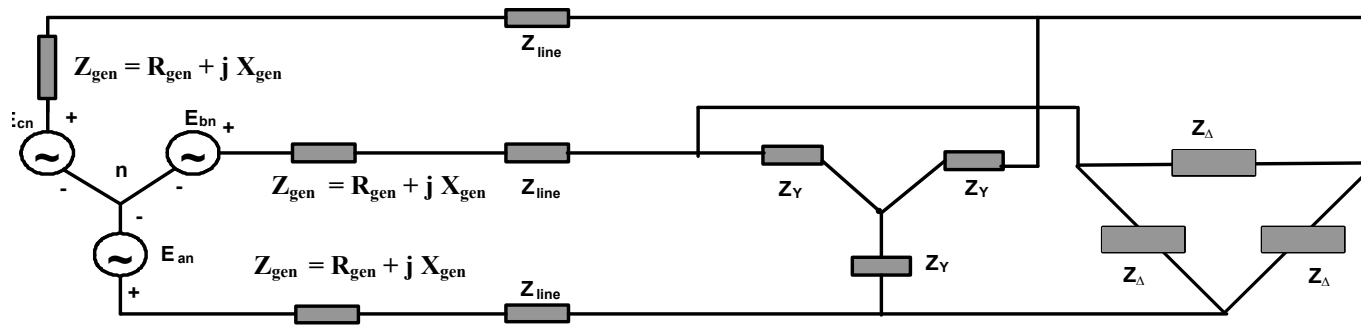The 3-phase system can supply two loads, one is delta connected and one is wye connected




Three Phase: balanced Circuit

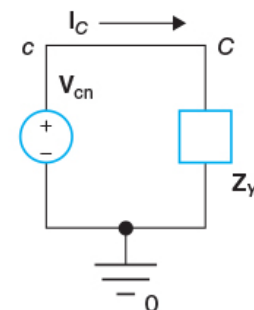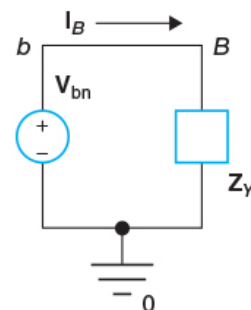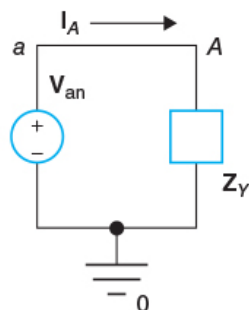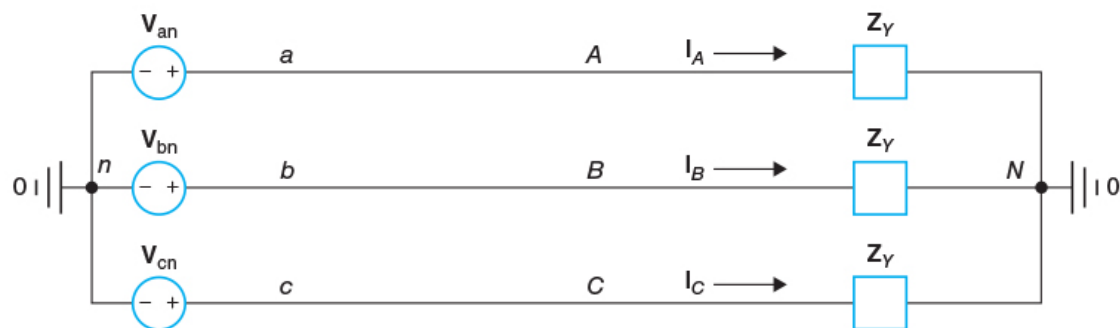- A balanced Y-connected source connected to the balanced Y-connected load is shown



Three Phase: Example 1

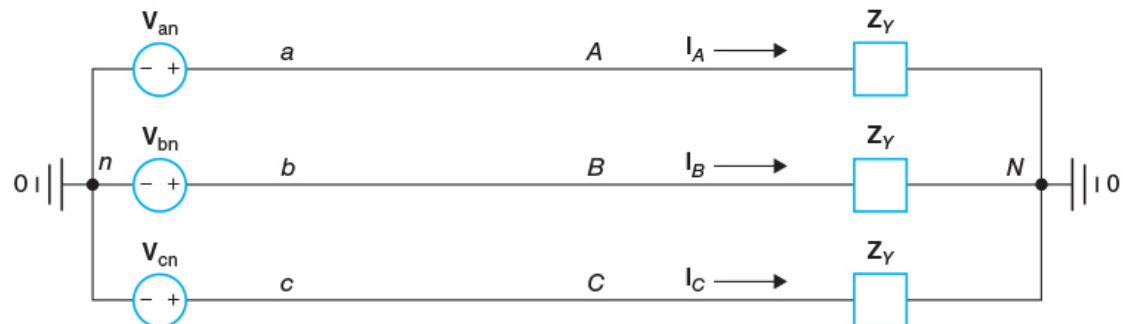- In the balanced Y-Y connection shown in Figure 12.6, let the magnitude of the line voltages be $V_L = 880 \text{ V (rms)}$, the load impedance per phase be $Z_Y = 50 + j25 \text{ Ohms}$, and the phase angle of V_{an} be 0° . Find the phase voltages, the line currents, and the line voltages. Also, find the complex power, apparent power, average power, reactive power, and power factor of the load.



Three Phase: Example 1 Solution

Three Phase: Example 2


- A balanced three-phase Y-connected generator with a positive sequence has an impedance of $0.2 + j0.5$ Ohms per phase and an internal voltage of 120 V/phase. The generator feeds a balanced three-phase Y-connected load having an impedance of $39 + j28$ Ohm per phase. The impedance of the line connecting the generator to the load is $0.8 + j1.5$ Ohm/phase. The a-phase internal voltage of the generator is specified as the reference phasor.
- A) construct the a-phase equivalent circuit of the system
- Calculate the three line currents
- Calculate the three-phase voltage at the load
- Calculate the line voltage at the terminal of the load
- Calculate the phase voltage at the terminal of the generator
- Calculate the line voltage at the terminal of the generator

Three Phase: Example 2 Solution



Three Phase: Complex Power

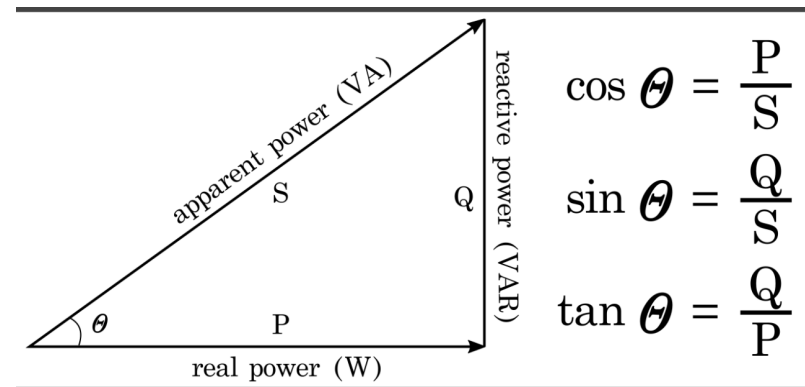- In a three-phase system, the total power is the sum of the three-phase power.
 - Under this section, the materials cover the followings
 - A) Complex power S
 - B) Real Power P
 - C) Reactive Power Q
-
- $S = \sqrt{3}V_L I_L^*$
 - $S = 3V_\phi I_\phi^*$
 - $P = S \times \text{Pf}$
 - $Q = S \times \sin(\theta)$



Three Phase: Example 3

- In a balanced three-phase system, the source has an abc sequence, is Y-connected, and $V_{an} = 120/20^\circ \text{ V}$. The source feeds two loads, both of which are Y-connected. The impedance of load 1 is $8 + j6 \text{ Ohms/phase}$. The complex power for the a-phase of load 2 is $600/36^\circ \text{ VA}$. Find the total complex power supplied by the source.

Three Phase: Example 3 Solution


Three Phase: Example 4

- A balanced three-phase source is supplying 60 kVA at 0.6 lagging to two balanced Y-connected parallel loads. The distribution line connecting the source to the load has negligible impedance. Load 1 is purely resistive and absorbs 30 kW. Find the per-phase impedance of Load 2 if the line voltage is 120 V and the impedance components are in series.

Three Phase: Example 4 Solution

Three Phase: Example 5

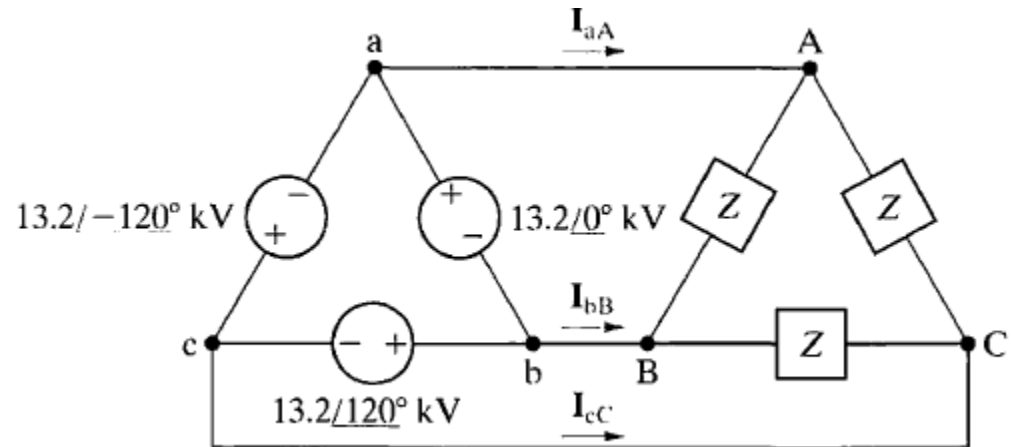- The impedance Z has the following value: $100 - j75$ Ohm. Finds the line current I_{aA} , I_{AB} and I_{bc} .



Three Phase: Example 5 Solution

Three Phase: Example 6

- A balanced, three-phase circuit is characterized as follows:
 - • Y-A connected;
 - • Source voltage in the c-phase is 20 and -90° V;
 - • Source phase sequence is abc;
 - • Line impedance is $1 + j3$ Ohms/Phase
 - • Load impedance is $117 - j99$ Ohms/Phase.
- a) Draw the single-phase equivalent for the a-phase.
- b) Calculate the a-phase line current.
- c) Calculate the a-phase line voltage for the three-phase load.

Three Phase: Example 6 Solution